

## 6.776 Final Project – 1.8GHz CMOS Transceiver


Nathan Monroe

[monroe@mit.edu](mailto:monroe@mit.edu)

5/13/2016

### Specifications

	Specified	This Design	Notes
Center Frequency	1.8GHz	1.8GHz	
$S_{11}$	-10dB min	-10.95dB min	1.7-1.9GHz
Voltage Gain	20dB	21.55dB	RF to IF
Noise Figure	6dB	3.7dB	100MHz
Power	30mW	24.1mW	
Bonus: Phase Noise	-120dBc/Hz	-127.7dBc/Hz	At $f_d = 600\text{KHz}$

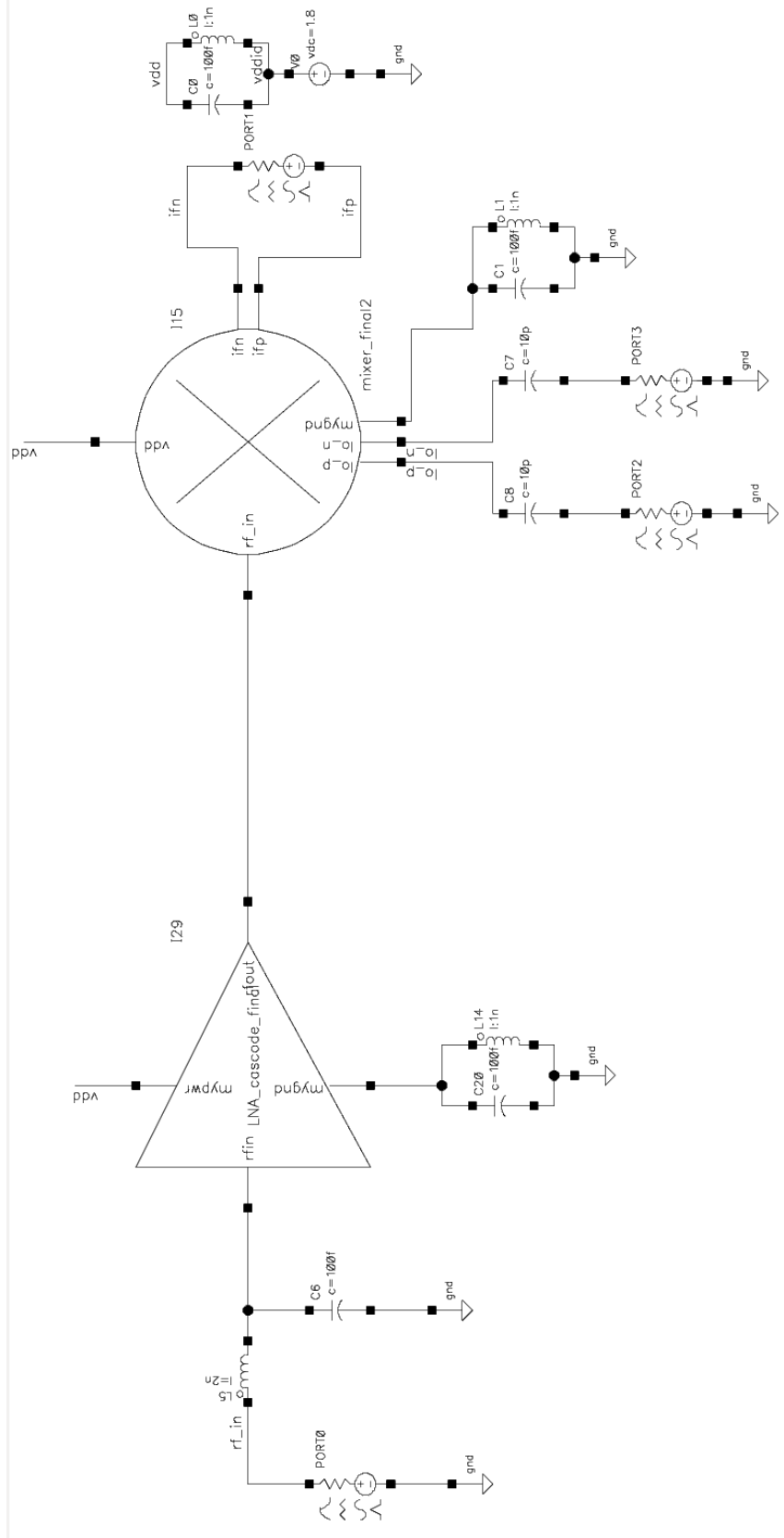


# LNA Design Discussion


Power Gain	Noise Figure	S11	Kf	Power
17.67dB	2.03dB	-11.92dB	1.99 min	8.76mW

The LNA subcomponent was redesigned from the previously submitted design. The new Cascode-based design has numerous advantages. First, it is a much smaller and more elegant design, yielding significant area savings over previous 2-stge designs. In addition, the use of a single stage reduces power significantly, while improving power gain and stability. The amplifier was designed using principles discussed in class, using inductive degeneration for simultaneous noise and impedance matching for optimal S11 and noise figure. The output was assumed to drive a 500 ohm plus 200fF load, representing the mixer input. The LNA's output inductor was designed to resonate with the load capacitance for optimal S22 matching. The real mixer load was found to be slightly lower capacitance, so the LNA inductor was tuned accordingly. See below for LNA schematic and test results.


LNA schematic

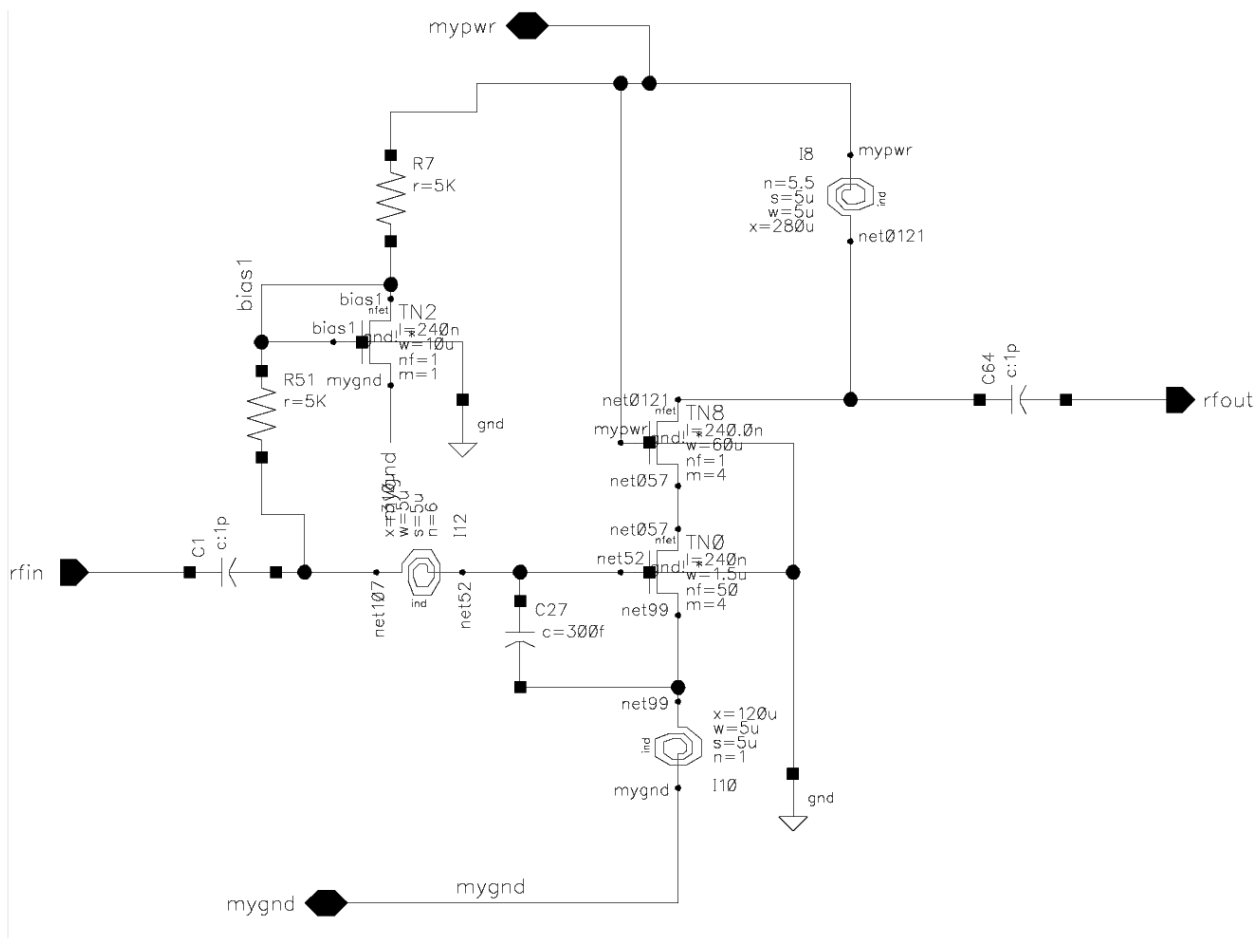


## LNA Gain, Kf, Noise Figure

 

## LNA Input/Output S parameters

 

## LNA Power

 


## Oscillator Design Discussion


Frequency	Power	Phase Noise (600KHz)	Output Swing
1.7GHz	6.6mW	-127.7dBc/Hz	3.2V (differential)

The Oscillator was also redesigned from previously submitted to improve performance. The redesign is also based on the cross-coupled oscillator, based on design principles discussed in lecture and in previous submissions. The redesign improves phase noise, power and output swing while sacrificing tunability. The design was based on the assumption of a 150fF load, representing the gate capacitance of the mixer. The mixer's gate capacitance was found to be 56fF, therefore the system was tuned during integration. See below for oscillator schematic and test results.


# Oscillator Schematic

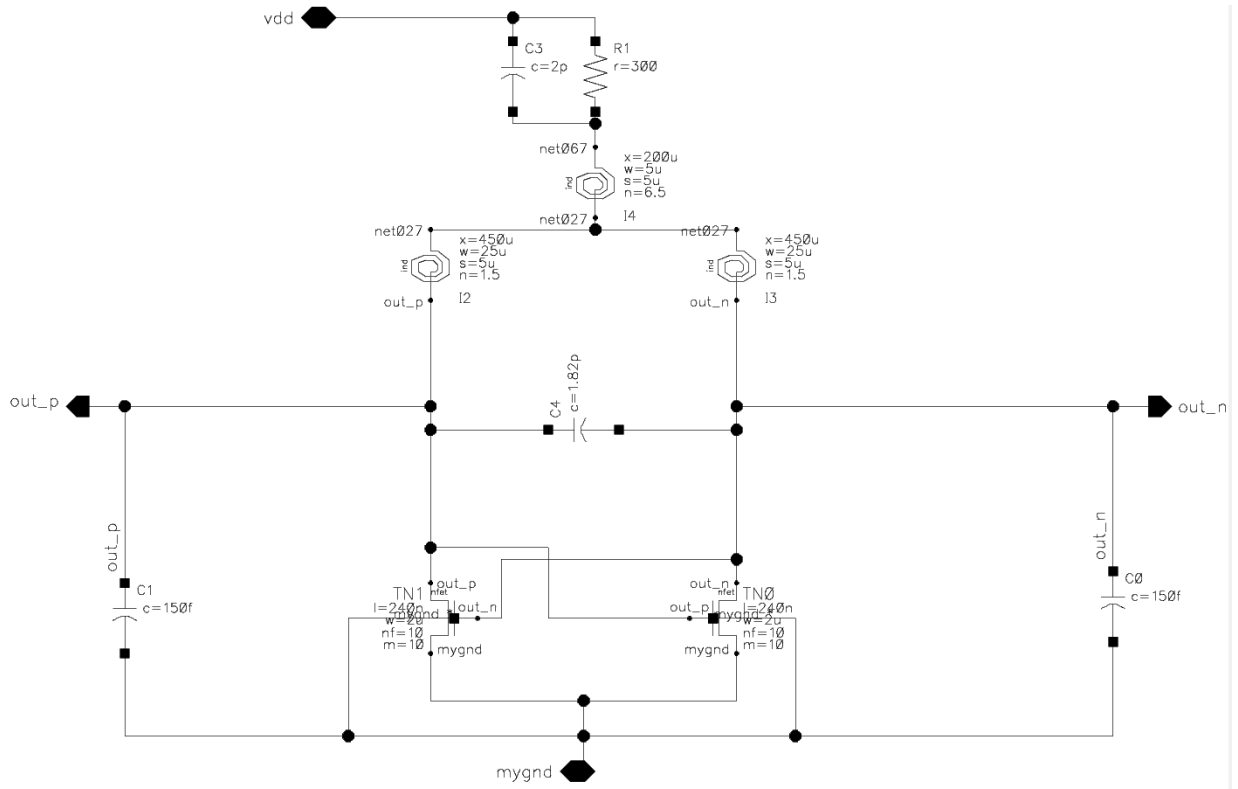


# Oscillator output

 

# Oscillator Phase Noise

 

# Oscillator Power

 


# Mixer Design Discussion

Voltage Gain	Power	Noise Figure
13.7dB	8.71mW (includes output buffer)	6.01dB


The mixer design was based on a single-balanced Gilbert cell mixer, consisting of a common source transconductance stage driven by RF input, and a switching stage driven by the LO input. The mixer stage itself consumes ~2mA. The mixer drives a differential NMOS source follower stage, which is used to drive the 50 ohm (100 ohm differential) outputs. The large Gm required to drive the low load impedance mandated large current in the output buffer stage of roughly 1.2mA per leg. A large Gm in the mixing stage allows for large gain, some of which is sacrificed in the output buffer stage due to heavy output loading. The choice of single balanced gilbert cell eliminates the need for a differentially-driven RF port and allows for low power consumption and simplistic design, but has the downside of large LO feedthrough to both RF and IF ports. Feedthrough to RF port results in self-mixing and a DC component to the output. The mixer transistors are biased with current mirror transistors, sized for minimum power draw.

## Mixer schematic

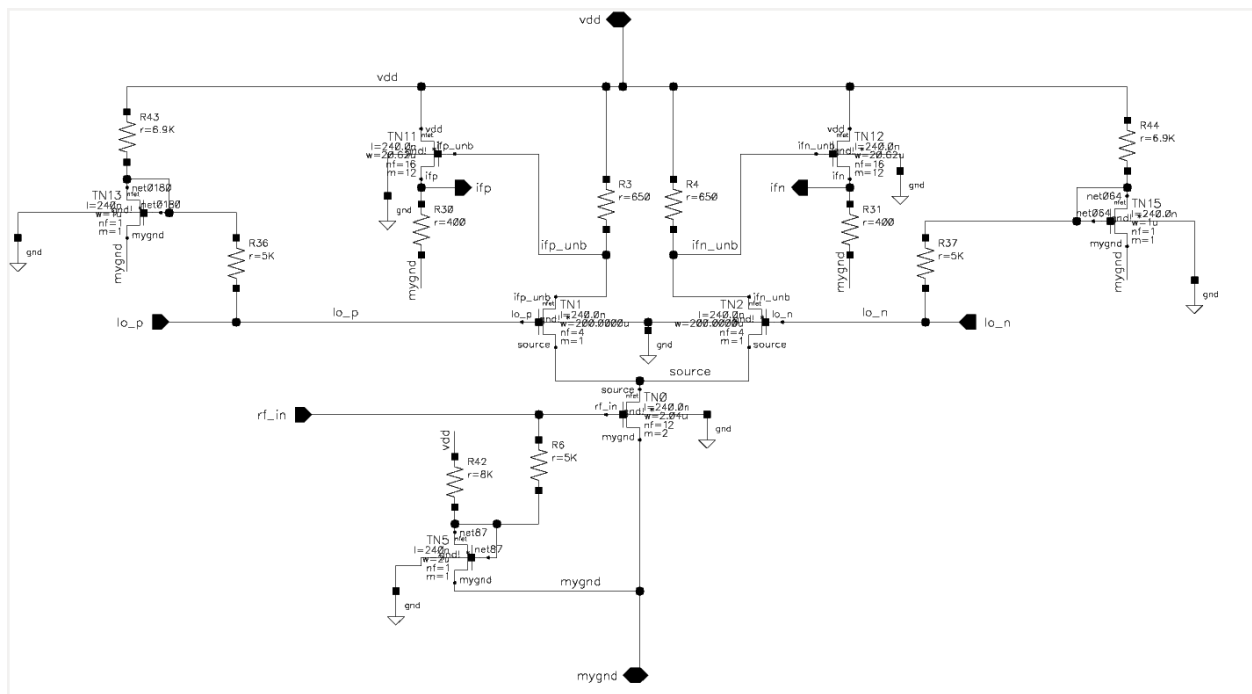





## Mixer Testbench

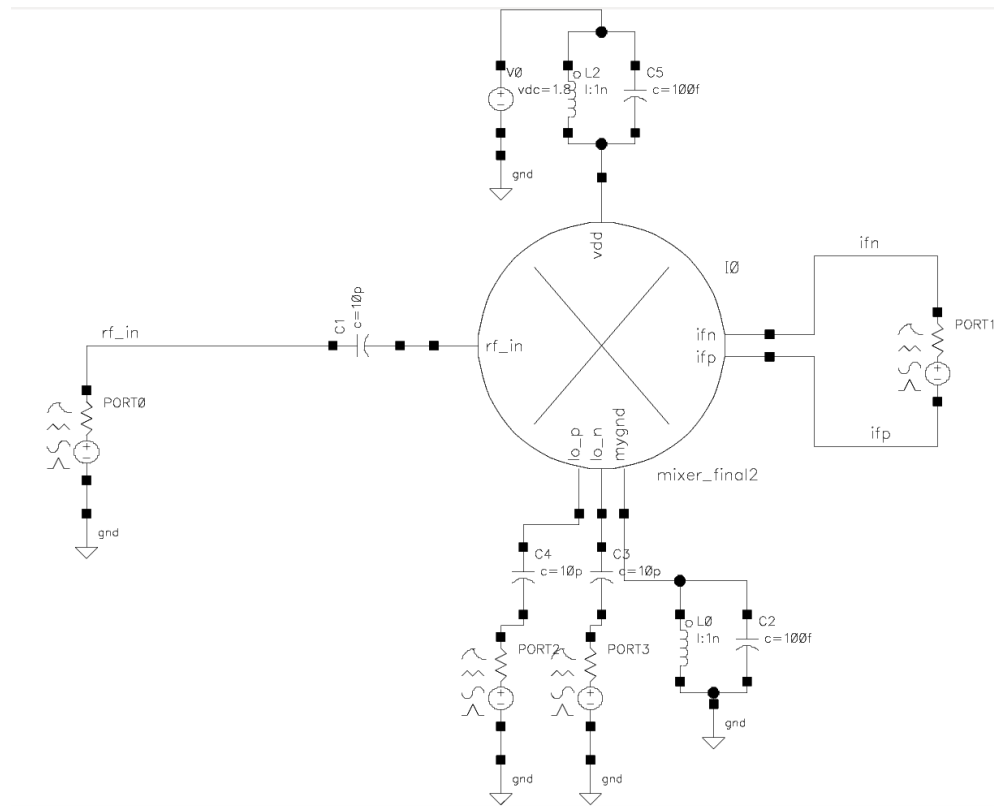


## Mixer gain

 

# Mixer Noise Figure

 

 
# Mixer Power Consumption (with output buffer)




## System Integration Discussion

After designing all subcomponents with proper loading assumption, system integration was relatively straightforward. The final value of gate capacitance load for the oscillator was found to be 56fF, so additional loading of 94fF was added to correct oscillation frequency based on design assumption of 150fF load for proper oscillation frequency. In addition, output and input inductances of the LNA were tuned to account for differences in loading than were predicted during design time. Ground bounce caused by high  $di/dt$  switching currents in the mixer through parasitic bondwire inductance was found to cause an unexpected instability in the LNA, leading to PSS convergence issues in Cadence. This was corrected by the addition of a separate grounding bondwire for the LNA. Due to the high gain of the system, noise figure came well within specification despite high NF of the mixing stage. The cascode architecture of the LNA yielded significant power savings, resulting in power consumption well below specification. The output buffer stage could have perhaps been tuned for reduced power and gain improvement, however both of these were within specification. Because the output buffer is driving a differential load, no coupling capacitors were necessary, saving cost. At IF frequencies of 100MHz, such capacitors would be large and costly.

### System gain and S11

 

## System noise figure

 

## References

<http://www.doe.carleton.ca/~jrogers/Bi.pdf>

[https://www.researchgate.net/publication/264396977\\_Design\\_and\\_Characterization\\_of\\_CMOS\\_Gilbert\\_Mixer\\_at\\_130\\_nm\\_Technology\\_for\\_Impedance\\_Measurement\\_System\\_of\\_Human\\_Cell\\_in\\_Institute\\_of\\_Nanoelectronics#pf36](https://www.researchgate.net/publication/264396977_Design_and_Characterization_of_CMOS_Gilbert_Mixer_at_130_nm_Technology_for_Impedance_Measurement_System_of_Human_Cell_in_Institute_of_Nanoelectronics#pf36)

<http://www.eecs.umich.edu/courses/eecs522/w11/project/group8report.pdf>

[https://filebox.ece.vt.edu/~symort/rfworkshop/Mixer\\_workshop\\_instruction.pdf](https://filebox.ece.vt.edu/~symort/rfworkshop/Mixer_workshop_instruction.pdf)

<https://hal.inria.fr/hal-00947369/document>